Linear Integrated Circuit <u>Lab</u>

Kabir 2K19/EE/130

Wien Bridge Oscillator

Aim


To simulate the output of Wien Bridge Oscillator using op-amp.

Software Used

LTspice.

Theory

LTspice Model

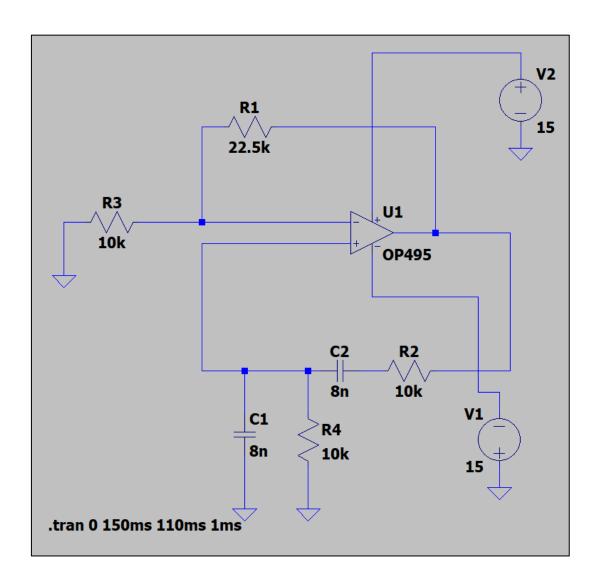

Observation

