

Linear Integrated Circuit

Lab

Kabir
2K19/EE/130

Astable Multivibrator

Aim


To simulate the output of Schmitt trigger using op-amp from a sinusoidal input.

Software Used

LTspice.

Theory

LTspice Model

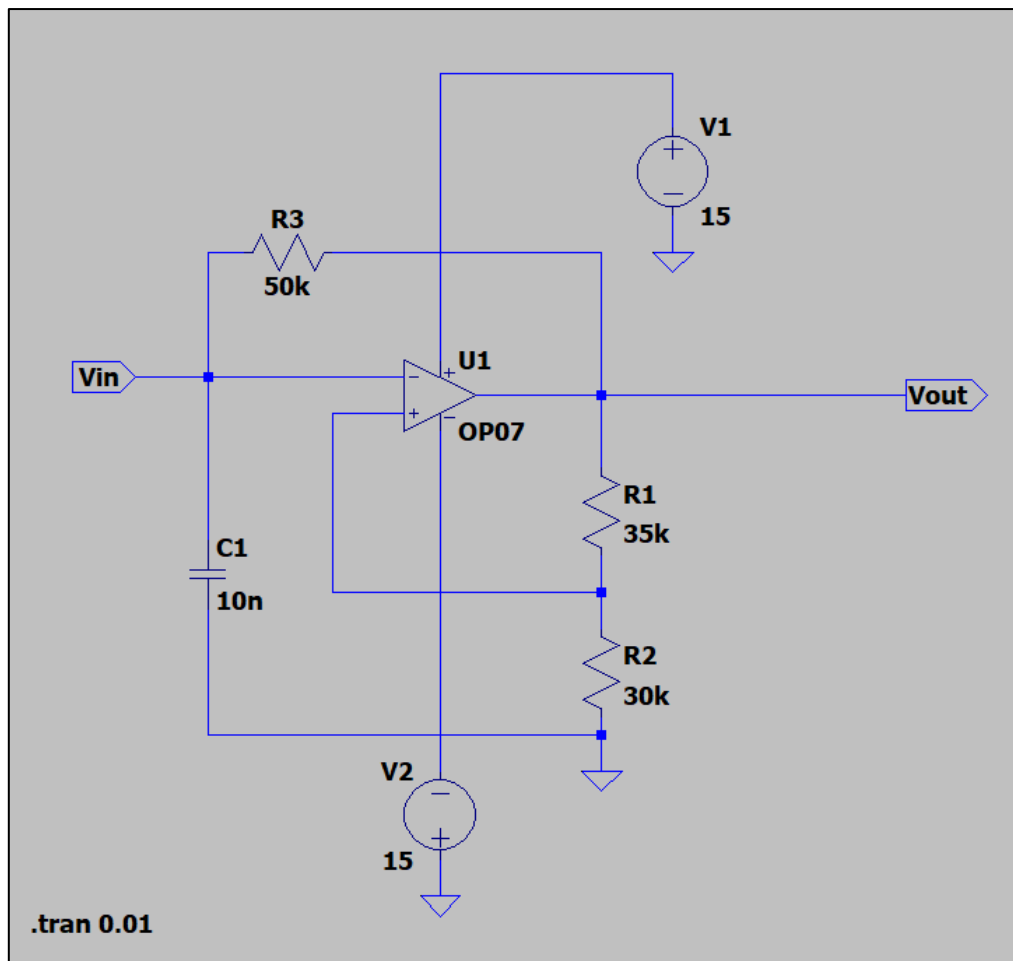

Observation

